

ECE212 Cheat Sheet

Stephen Yang

December 2020

1 Circuit Analysis


1.1 Ohm's Law

$$V = IR$$

1.2 Linearity Property


$$kiR = kv$$

1.3 Voltage Divider

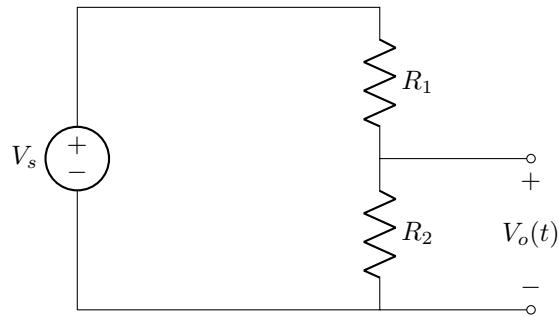

$$V_o = \frac{R_2}{R_1 + R_2} V_s$$

1.4 Current Divider

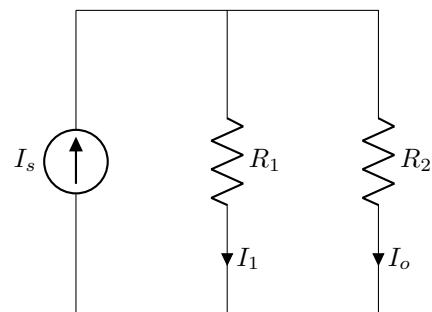

$$I_o = \frac{R_1}{R_1 + R_2} I_s$$

2 Operational Amplifiers

2.1 Ideal OpAmp Characteristics


- $R_{in} \rightarrow \infty \Rightarrow i_N, i_P = 0$
- $R_{out} \rightarrow 0 \Rightarrow V_{out} = A(V_P - V_N)$
- $A \rightarrow \infty$

2.2 Ideal OpAmp Properties

- $V_P = V_N$
- $i_P = 0$
- $i_N = 0$
- Circuit is balanced ($R_{out} = 0$)

3 Element Constraints

3.1 Current Source

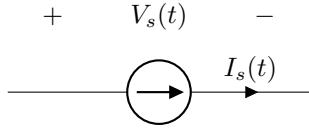

3.1.1 Time Domain

$$I_s(t) = I_m \cos(\omega t + \theta_s)$$


3.1.2 Frequency/Complex Domain

$$\bar{I}_s = I_m e^{j\theta_s}$$

3.1.3 S/Laplace Domain

$$I_s(s) = \mathcal{L}\{I_s(t)\}(s)$$

3.2 Voltage Source

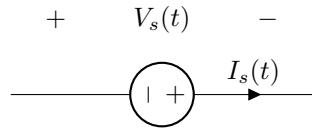

3.2.1 Time Domain

$$V_s(t) = V_m \cos(\omega t + \theta_s)$$

3.2.2 Frequency/Complex Domain

$$\bar{V}_s = V_m e^{j\theta_s}$$

3.2.3 S/Laplace Domain

$$V_s(s) = \mathcal{L}\{V_s(t)\}(s)$$

3.3 Resistors



$$V = iR$$

3.4 Inductors



3.4.1 Time Domain

$$V_L = L \frac{di}{dt}$$

$$i_L = \frac{1}{L} \int_0^t V_L(t) dt + i_L(0)$$


3.4.2 Frequency/Complex Domain

$$V_L(j\omega) = j\omega L I_L$$

3.4.3 S/Laplace Domain

$$V_L(s) = s L I_L$$

3.5 Capacitors

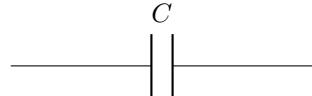

$$i_C = C \frac{dv}{dt}$$

$$V_C = \frac{1}{C} \int_0^t i_C(t) dt + i_C(0)$$

3.5.1 Frequency/Complex Domain

$$V_C(j\omega) = \frac{1}{j\omega C} I_C$$

3.5.2 S/Laplace Domain

$$V_C(s) = \frac{1}{sC} I_C$$

4 Coupled Inductors and Transformers

4.1 Flux

$$\phi(t) = kN_1 i(t)$$

4.2 Flux Linkage

$$\lambda = N_1 \phi(t) = kN_1^2 i(t)$$

4.3 Voltage


Voltage across an inductor is given by

$$V(t) = \frac{d\lambda}{dt} = \frac{d}{dt} N_1 \phi(t) = kN_1^2 \frac{di}{dt}$$

Where

$$L = kN_1^2$$

4.4 Coupled Inductors

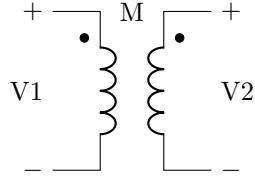

4.4.1 Time Domain

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$


$$v_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

4.4.2 Frequency/Complex Domain

$$\bar{V}_1 = j\omega L_1 \bar{I}_1 + j\omega M \bar{I}_2$$

$$\bar{V}_2 = j\omega M \bar{I}_1 + j\omega L_2 \bar{I}_2$$

4.5 Transformers

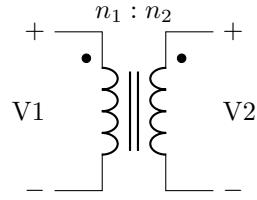

$$i_1 n_1 + i_2 n_2 + \dots + i_k n_k = 0$$

$$\frac{V_1}{n_1} = \frac{V_2}{n_2} = \dots = \frac{V_k}{n_k}$$

5 Complex Power

5.1 Complex Current/Voltage

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$\mathbf{V} = V_m \angle \theta_v \quad \mathbf{I} = I_m \angle \theta_i$$

5.2 Effective Value and RMS

The effective value of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current

For a given periodic function $x(t)$, the RMS value is

$$X_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2 dt}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$\mathbf{V}_{rms} = \frac{\mathbf{V}}{\sqrt{2}} = V_{rms} \angle \theta_v \quad \mathbf{I}_{rms} = \frac{\mathbf{I}}{\sqrt{2}} = I_{rms} \angle \theta_i$$

5.3 Instantaneous Power

$$p(t) = v(t)i(t)$$

$$p(t) = \frac{1}{2} V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

5.4 Average Power

$$P = \frac{1}{T} \int_0^T p(t) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P = \text{Re}[\frac{1}{2} \mathbf{V} \mathbf{I}^*]$$

$$P = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

5.5 Maximum Average Power Transfer

For a Thevenin equivalent circuit with impedance Z_{Th}

$$\mathbf{Z}_L = R_L + jX_L = R_{Th} - jX_{Th} = \mathbf{Z}_{Th}^*$$

5.6 Apparent Power

$$S = V_{rms} I_{rms}$$

$$S = |\mathbf{S}| = |\mathbf{V}_{rms}| |\mathbf{I}_{rms}|$$

$$S = \sqrt{P^2 + Q^2}$$

5.7 Power Factor

$$\text{pf} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

- Unity Power Factor
 - $Q = 0$
 - Purely resistive loads
- Leading Power Factor
 - $Q < 0$
 - Capacitive loads
- Lagging Power Factor
 - $Q > 0$
 - Inductive loads

5.8 Complex Power

Units: VA

$$\mathbf{S} = P + Qj$$

$$\mathbf{S} = |\mathbf{V}_{rms}| |\mathbf{I}_{rms}| \angle \theta_v - \theta_i$$

$$\mathbf{S} = \frac{1}{2} \mathbf{VI}^* = \mathbf{V}_{rms} \mathbf{I}_{rms}^*$$

$$\mathbf{S} = I_{rms}^2 \mathbf{Z} = \frac{V_{rms}^2}{\mathbf{Z}^*} = \mathbf{V}_{rms} \mathbf{I}_{rms}^*$$

5.9 Real Power

Also known as Active, or Average Power

Units: W

$$P = \text{Re}(\mathbf{S}) = S \cos(\theta_v - \theta_i)$$

5.10 Reactive Power

Also known as Complex, or Imaginary Power

Units: VA_R

$$Q = \text{Im}(\mathbf{S}) = S \sin(\theta_v - \theta_i)$$

6 Frequency Response

6.1 Transfer Functions

For a specific phasor input/output pair $X(s)$ and $Y(s)$, and $s = j\omega$

$$T(s) = \frac{Y(s)}{X(s)} = \frac{\mathcal{L}\{y(t)\}(s)}{\mathcal{L}\{x(t)\}(s)}$$

$X(s)$ and $Y(s)$ are the laplace transforms of time domain signals, such as voltage or current

6.2 Transfer Function Examples

| | |
|---------------------|--------------------------------|
| Voltage Gain | $H(s) = \frac{V_o(s)}{V_i(s)}$ |
| Current Gain | $H(s) = \frac{I_o(s)}{I_i(s)}$ |
| Transfer Impedance | $H(s) = \frac{V_o(s)}{I_i(s)}$ |
| Transfer Admittance | $H(s) = \frac{I_o(s)}{V_i(s)}$ |

6.3 Gain

Gain is measured in **decibels**

$$G_{dB} = 10 \log_{10} \left(\frac{P_1}{P_2} \right)$$

Assuming $R_1 = R_2$ and using $P = IV = \frac{V^2}{R} = I^2R$

$$G_{dB} = 20 \log_{10} \left(\frac{V_1}{V_2} \right)$$

$$G_{dB} = 20 \log_{10} \left(\frac{I_1}{I_2} \right)$$

6.4 Bode Plot Features

| Factor | Function | Gain | Phase |
|---------------------------|-------------------------------|------------------------------------|---|
| Constant | K | $20 \log_{10}(K)$ | 0° if $k > 0$, else 180° |
| Zero at Origin | $j\omega$ | $20 \log_{10}(\omega)$ | 90° |
| Pole at Origin | $\frac{1}{j\omega}$ | $-20 \log_{10}(\omega)$ | -90° |
| Zero at Origin of Order N | $(j\omega)^N$ | $20N \log_{10}(\omega)$ | $90N^\circ$ |
| Pole at Origin of Order N | $\frac{1}{(j\omega)^N}$ | $-20N \log_{10}(\omega)$ | $-90N^\circ$ |
| Simple Zero | $(1 + j\omega/z_1)$ | $20 \log_{10} 1 + j\omega/z_1 $ | $\tan^{-1}(\frac{\omega}{z_1})$ |
| Simple Pole | $\frac{1}{1+j\omega/z_1}$ | $-20 \log_{10} 1 + j\omega/z_1 $ | $-\tan^{-1}(\frac{\omega}{z_1})$ |
| Zero of Order N | $(1 + j\omega/z_1)^N$ | $20N \log_{10} 1 + j\omega/z_1 $ | $N \tan^{-1}(\frac{\omega}{z_1})$ |
| Pole of Order N | $\frac{1}{1+(j\omega/z_1)^N}$ | $-20N \log_{10} 1 + j\omega/z_1 $ | $-N \tan^{-1}(\frac{\omega}{z_1})$ |

7 Trig Identities

7.1 Trigonometric Functions

For any complex number $z = x + iy$

$$\sin(z) = \frac{e^{iz} - e^{-iz}}{2i} \quad \cos(z) = \frac{e^{iz} + e^{-iz}}{2}$$

$$\frac{d}{dz} \sin(z) = \cos(z) \quad \frac{d}{dz} \cos(z) = -\sin(z)$$

7.2 Trig Identities

$$\left| \begin{array}{l} \tan(x) = \frac{\sin(x)}{\cos(x)} \\ \sec(x) = \frac{1}{\cos(x)} \end{array} \right| \left| \begin{array}{l} \csc(x) = \frac{1}{\sin(x)} \\ \cot(x) = \frac{\cos(x)}{\sin(x)} \end{array} \right|$$

$$\sin^2(x) = \frac{1 - \cos(2x)}{2}$$

$$\cos^2(x) = \frac{1 + \cos(2x)}{2}$$

$$\tan^2(x) = \frac{1 - \cos(2x)}{1 + \cos(2x)}$$

$$\sin(2x) = 2 \sin(x) \cos(x)$$

$$\cos(2x) = \cos^2(x) - \sin^2(x)$$

$$\cos(2x) = 2 \cos^2(x) - 1$$

$$\cos(2x) = 1 - 2 \sin^2(x)$$

$$\sin(x + y) = \sin(x) \cos(y) + \sin(y) \cos(x)$$

$$\cos(x + y) = \cos(x) \cos(y) - \sin(x) \sin(y)$$

7.3 Hyperbolic Trig Functions

For any complex number $z = x + iy$

$$\sinh(x) = \frac{e^x - e^{-x}}{2} \quad \cosh(x) = \frac{e^x + e^{-x}}{2}$$

$$\frac{d}{dz} \sinh(z) = \cosh(z) \quad \frac{d}{dz} \cosh(z) = \sinh(z)$$

7.4 Hyperbolic Trig Identities

$$\left| \begin{array}{l} \tanh(z) = \frac{\sinh(z)}{\cosh(z)} \\ \operatorname{sech}(z) = \frac{1}{\cosh(z)} \end{array} \right| \left| \begin{array}{l} \operatorname{csch}(z) = \frac{1}{\sinh(z)} \\ \coth(z) = \frac{\cosh(z)}{\sinh(z)} \end{array} \right|$$

$$\sinh(-z) = -\sinh(z)$$

$$\cosh(-z) = \cosh(z)$$

$$\cosh^2(z) - \sinh^2(z) = 1$$

$$1 - \tanh^2(z) = \operatorname{sech}^2(z)$$

$$\sinh(x + y) = \sinh(x) \cosh(y) + \cosh(x) \sinh(y)$$

$$\cosh(x + y) = \cosh(x) \cosh(y) + \sinh(x) \sinh(y)$$

$$\sin(z) = \sin(x) \cosh(y) + i \cos(x) \sinh(y)$$

$$\cos(z) = \cos(x) \cosh(y) - i \sin(x) \sinh(y)$$

8 Differential Equations

8.1 Solution Types for Homogenous 2nd Degree Linear ODE's

For an ODE of the form:

$$ay'' + by' + c = 0$$

and characteristic/auxiliary polynomial:

$$ar^2 + br + c = 0$$

with roots

$$r_1 = \frac{-b - \sqrt{b^2 - 4ac}}{2a} \quad r_2 = \frac{-b + \sqrt{b^2 - 4ac}}{2a}$$

8.1.1 Distinct Roots - Overdamped

$$y_h = c_1 e^{r_1 t} + c_2 e^{r_2 t}$$

8.1.2 Repeated Roots - Critically Damped

e.g. $r_1 = r_2 = r$

$$y_h = c_1 e^{rt} + c_2 t e^{rt}$$

8.1.3 Complex Conjugate Roots - Underdamped

If r_1, r_2 complex, then we can write $r_1 = a + ib, r_2 = a - ib$

$$y_h = e^{ax} (c_1 \cos(bx) + c_2 \sin(bx))$$

9 Laplace Transform

Let f be a function defined for $t \geq 0$

$$\mathcal{L}\{f(t)\} = \int_0^\infty e^{-st} f(t) dt$$

9.1 Basic Laplace Transforms

$$\left| \begin{array}{ll} \mathcal{L}\{1\} = \frac{1}{s} & \mathcal{L}\{t^n\} = \frac{n!}{s^{n+1}} \\ \mathcal{L}\{\sin(kt)\} = \frac{k}{s^2 + k^2} & \mathcal{L}\{\cos(kt)\} = \frac{s}{s^2 + k^2} \\ \mathcal{L}\{\sinh(kt)\} = \frac{k}{s^2 - k^2} & \mathcal{L}\{\cosh(kt)\} = \frac{s}{s^2 - k^2} \end{array} \right|$$

9.2 First Translation Theorem

If $\mathcal{L}\{f(t)\} = F(s)$ and a is any real number, then

$$\mathcal{L}\{e^{at}f(t)\}(s) = \mathcal{L}\{f(t)\}(s - a) = F(s - a)$$

9.3 Second Translation Theorem

The **unit step function** $u(t - a)$ is defined as

$$u(t - a) = \begin{cases} 0 & \text{if } 0 \leq t < a \\ 1 & \text{if } t \geq a \end{cases}$$

If $\mathcal{L}\{f(t)\} = F(s)$ and $a > 0$, then

$$\mathcal{L}\{f(t - a)u(t - a)\} = e^{-as}F(s)$$

9.4 Transforms of Derivatives

If $f, f', \dots, f^{(n-1)}$ are continuous on $[0, \infty)$ and are of exponential order, and if $f^{(n)}(t)$ is piecewise continuous on $[0, \infty)$, then

$$\mathcal{L}\{f^{(n)}(t)\} = s^n F(s) - s^{n-1}f(0) - s^{n-2}f'(0) - \dots - f^{(n-1)}(0)$$

where $F(s) = \mathcal{L}\{f(t)\}$

$$\mathcal{L}\{f''(t)\} = s^2 F(s) - sf(0) - f'(0)$$

$$\mathcal{L}\{f'(t)\} = sF(s) - f(0)$$

9.5 Derivatives of Transforms

If $\mathcal{L}\{f(t)\} = F(s)$ and $n = 1, 2, 3, \dots$, then

$$\mathcal{L}\{t^n f(t)\} = (-1)^n \frac{d^n}{ds^n} F(s)$$

9.6 Transform of Integrals

$$\mathcal{L}\left\{\int_0^t f(\tau)d\tau\right\} = \frac{F(s)}{s}$$

$$\int_0^t f(\tau)d\tau = \mathcal{L}^{-1}\left\{\frac{F(s)}{s}\right\}$$

9.7 Convolution

9.7.1 Convolution Operation

If $f(t)$ and $g(t)$ are piecewise continuous on $[0, \infty)$, then the **convolution** of f and g , denoted by the symbol $f * g$, is

$$f * g = \int_0^t f(\tau)g(t - \tau)d\tau$$

9.7.2 Convolution Theorem

If $f(t)$ and $g(t)$ are piecewise continuous on $[0, \infty)$ and of exponential order, then

$$\mathcal{L}\{f * g\} = \mathcal{L}\{f(t)\} \mathcal{L}\{g(t)\} = F(s)G(s)$$

9.7.3 Convolution in Inverse

$$\mathcal{L}^{-1}\{F(s)G(s)\} = f * g$$

9.8 Dirac Delta Function

9.8.1 Unit Impulse

$$\delta_a(t - t_0) = \begin{cases} 0 & \text{if } 0 \leq t < t_0 - a \\ \frac{1}{2a} & \text{if } t_0 + a \leq t \leq t_0 + a \\ 0 & \text{if } t \geq t_0 + a \end{cases}$$

9.8.2 Dirac Delta Definition

$$\delta(t - t_0) = \begin{cases} \infty & \text{if } t = t_0 \\ 0 & \text{if } t \neq t_0 \end{cases}$$

Area under the distribution is 1:

$$\int_{-\infty}^{\infty} \delta(x - a)dx = 1$$

Sampling/Shifting Property:

$$\int_{-\infty}^{\infty} f(x)\delta(x - a)dx = f(a)$$

9.8.3 Dirac Delta Transform

For $t_0 > 0$

$$\mathcal{L}\{\delta(t - t_0)\} = e^{-st_0}$$

$$\mathcal{L}\{\delta(t)\} = 1$$

9.9 Additional Laplace Properties

9.9.1 Transform of a Periodic Function

If $f(t)$ is

- is piecewise continuous on $[0, \infty)$
- of exponential order
- periodic with period T

$$\mathcal{L}\{f(t)\} = \frac{1}{1 - e^{-sT}} \int_0^T e^{-st} f(t) dt$$

9.9.2 Volterra Integral Equation

$$f(t) = g(t) + \int_0^t f(\tau)h(t - \tau)d\tau$$

Taking Laplace transform of both sides:

$$F(s) = G(s) + \mathcal{L}\{f(t) * h(t)\} = G(s) + F(s)H(s)$$

9.9.3 Integrodifferential Equation

Circuit Analogy:

$$L \frac{di}{dt} + Ri(t) + \frac{1}{C} \int_0^t i(\tau)d\tau = E(t)$$

10 Inverse Laplace Transforms

10.1 Basic Inverse Laplace Transforms

| | |
|---|---|
| $\mathcal{L}^{-1}\left\{\frac{1}{s}\right\} = 1$ $\mathcal{L}\left\{\frac{1}{s-a}\right\} = e^{at}$ $\mathcal{L}^{-1}\left\{\frac{k}{s^2+k^2}\right\} = \sin(kt)$ $\mathcal{L}^{-1}\left\{\frac{k}{s^2-k^2}\right\} = \sinh(kt)$ | $\mathcal{L}^{-1}\{1\} = \delta(t)$ $\mathcal{L}^{-1}\left\{\frac{n!}{s^{n+1}}\right\} = t^n$ $\mathcal{L}^{-1}\left\{\frac{s}{s^2+k^2}\right\} = \cos(kt)$ $\mathcal{L}^{-1}\left\{\frac{s}{s^2-k^2}\right\} = \cosh(kt)$ |
|---|---|